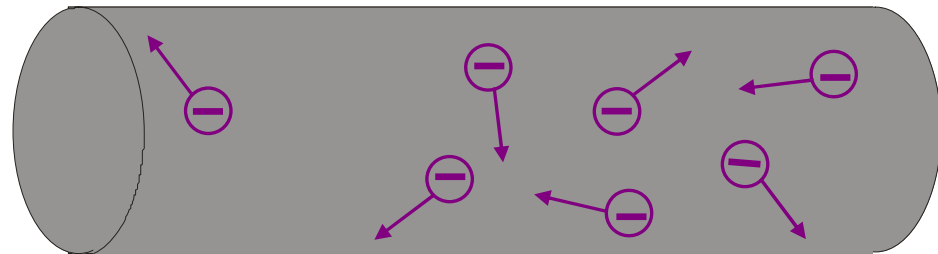




## ELECTRIC CURRENT

Electric current is a motion of charge from one region to another.

In metals some of the electrons are free to move within material. In the absence of electric field they move randomly in all directions with speed of the order of  $10^6$  m/s and undergo frequent collisions with the positive ions of the material. There is no net flow of charge in any direction.




When a steady electric field is established inside a conductor, there is a net motion or drift of charge in the direction of the electric force,

$$\vec{F} = q\vec{E}$$

The drift velocity  $\vec{V}_d$  of electrons in metal is very slow in comparison to their average speed ( $\sim 10^6$  m/s).

# ELECTRIC CURRENT

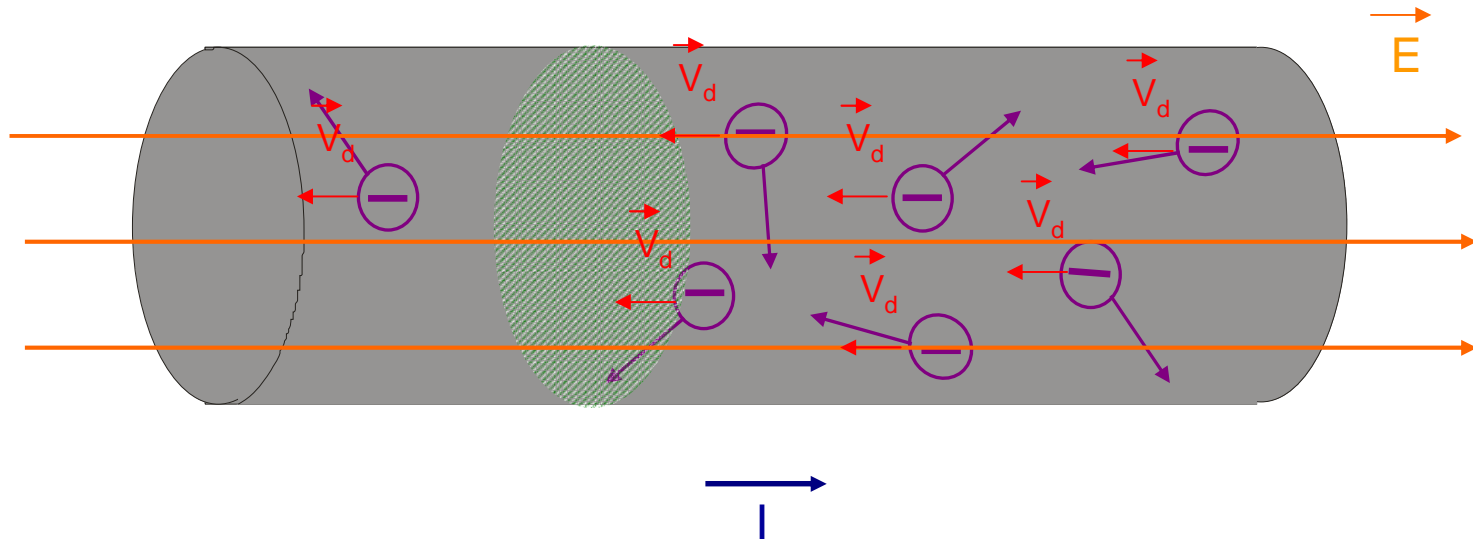

A current arrow indicates the direction in which positive charge carriers would move. The current ( $I$ ) is defined as the net charge flowing through the area per unit time:

$$I = \frac{dQ}{dt}$$

$$[I] = \frac{\text{coulomb}}{\text{second}} = \text{ampere}$$

## Electric current density in a conductor

If all charge move with  $V_d$  then during the time interval  $dt$  all particles move a distance  $V_d dt$ . They can cross the area  $A$  during the time interval  $dt$  if they are within the cylinder of the volume:

$$dV = A V_d dt$$

The total charge of moving charge particles in the volume  $dV$  is:

$$dQ = q n A V_d dt$$

where  $n$ - number of moving charge particles per unit volume.

So, the current is


$$I = q n A V_d$$

The current per unit cross-section area is called current density:

$$\mathbf{j} = \frac{I}{A} = q n \mathbf{V}_d$$


The current density is a vector quantity and its vector definition takes the form:

$$\vec{j} = q n \vec{V}_d$$

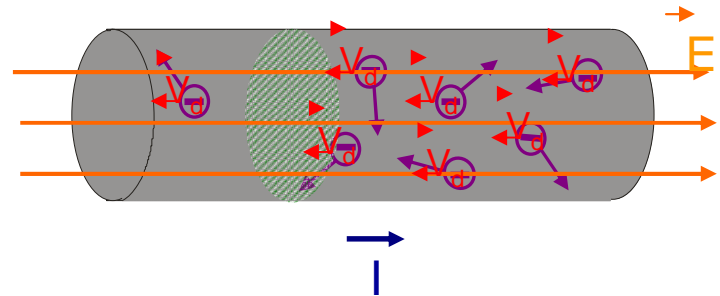
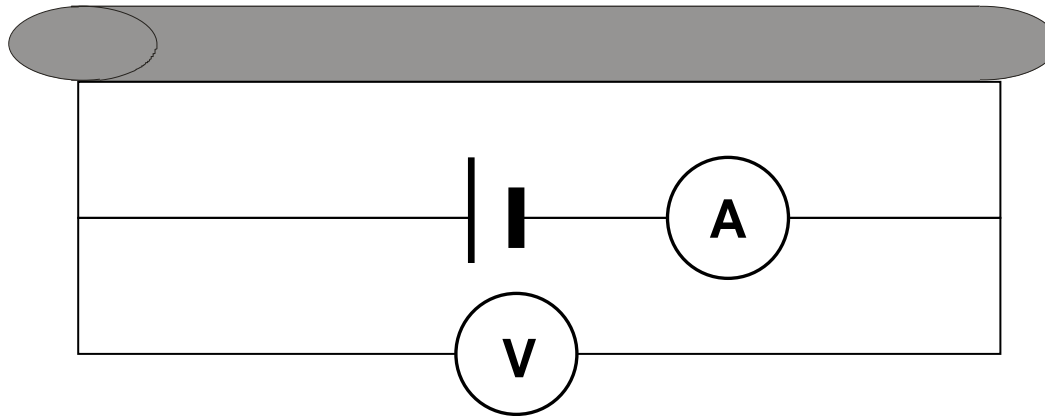
## Resistors and their resistance

In the case of metal the electric current at a given temperature is nearly directly proportional to an electric potential difference applied between any two points of metal.



The ratio of a potential difference to the electric current is then called resistance  $R$ :

$$R = \frac{V}{I}$$

$$[R] = \frac{V}{A} = \Omega$$

**George Simon Ohm (1787-1854)**

The resistance of a metal wire is proportional to its length ( $l$ ) and inversely proportional to its cross-section area ( $A$ ):

$$R = \rho \frac{l}{A} \quad [R] = \Omega \text{m}$$


where  $\rho$  is the resistivity of the material.

Using  $\rho$  we can write vector relation between  $\vec{E}$  and  $\vec{j}$  for resistor:

$$\vec{E} = \rho \vec{j}$$

The reciprocal of resistivity is known as conductivity ( $\sigma$ ):


$$\sigma = \frac{1}{\rho}$$

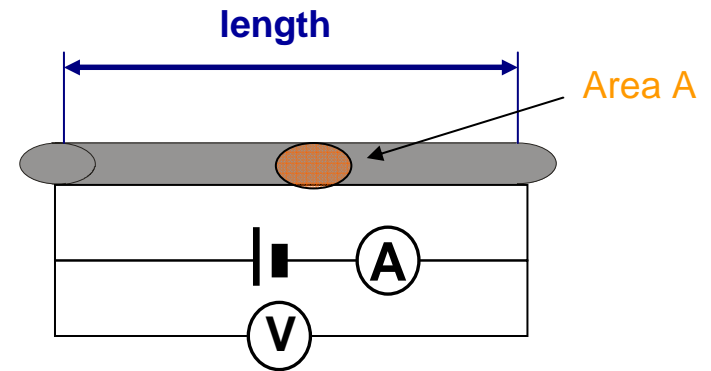

<i>material</i>	<i>resistivity at room temperature</i>
Silver	$1.62 \times 10^{-8} \Omega \text{ m}$
Copper	$1.69 \times 10^{-8} \Omega \text{ m}$
Gold	$2.35 \times 10^{-8} \Omega \text{ m}$
Aluminum	$2.75 \times 10^{-8} \Omega \text{ m}$


Current versus potential difference applied to:

a) a resistor,

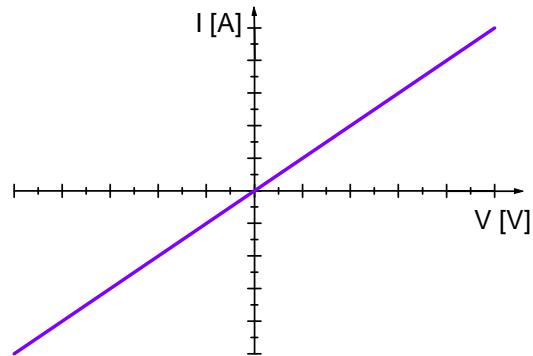

*A resistor obeys Ohm's Law*

b) a diode

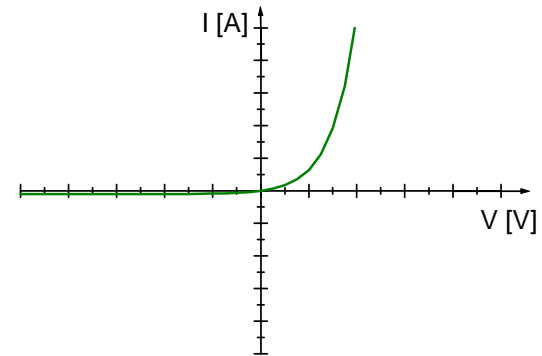

*A diode does not obey Ohm's Law*

## Electromotive force

An electromotive (emf) device is a device which maintains a potential difference between a pair of terminals by doing work on the charge carriers.

Electromotive force ( $\varepsilon$ ) is defined as:

$$\varepsilon = \frac{dW}{dq}$$

$$[\varepsilon] = \frac{\text{J}}{\text{C}} = \text{V}$$

joule per coulomb

volt


$dW$  – work done on the charge  $dq$  in moving it from low-potential terminal to high-potential terminal.

Emf devices:

- battery,
- electric generator,
- solar cells,
- fuel cells.

An emf device does work on the charge carriers to force them to move from low-potential end to high potential end.

## Multiloop circuit

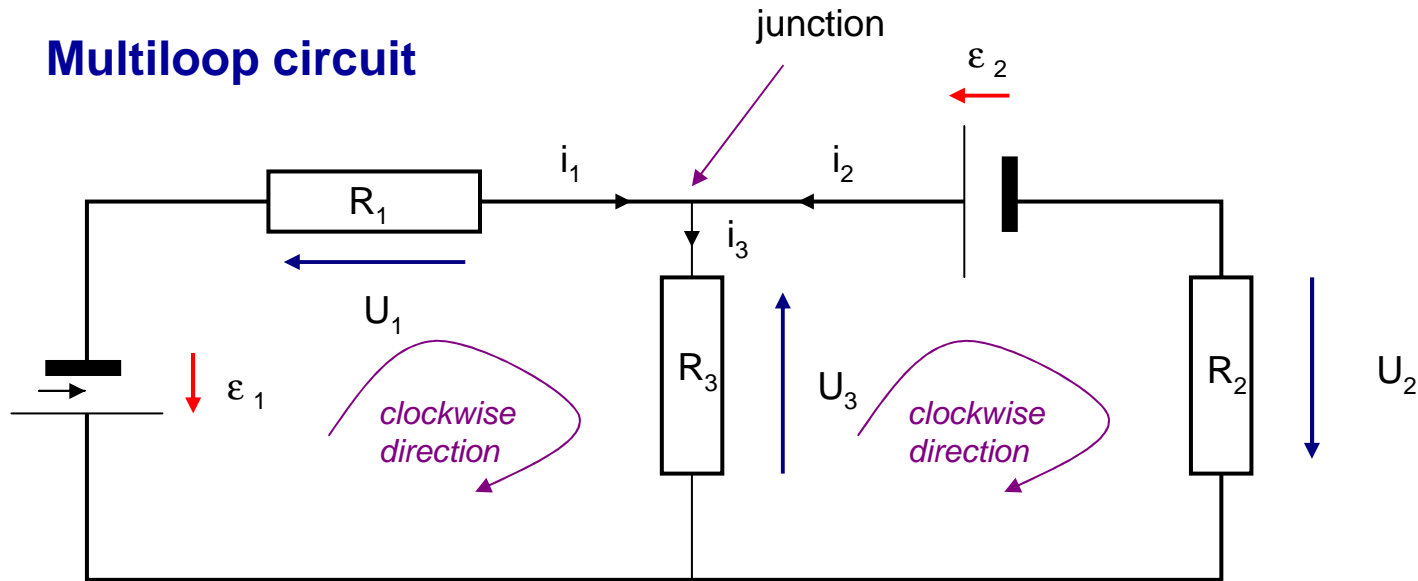

### Kirchhoff's junction rule

At any junction the algebraic sum of the currents must be zero.

$$\underbrace{i_1 + i_2}_{\text{currents approaching the junction}} - \underbrace{i_3}_{\text{current leaving the junction}} = 0$$

*currents approaching the junction*

*current leaving the junction*


### Kirchhoff's loop rule

The algebraic sum of the potential differences in any loop must equal zero.

$$-\varepsilon_1 - U_1 - U_3 = 0$$

$$U_3 - \varepsilon_2 + U_2 = 0$$

*for clockwise direction*

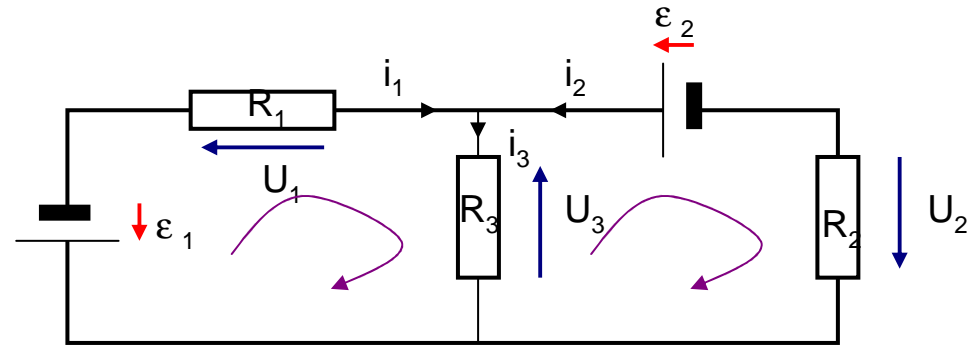

$$\left\{ \begin{array}{l} i_1 + i_2 - i_3 = 0 \\ -\varepsilon_1 - R_1 i_1 - R_3 i_3 = 0 \\ R_3 i_3 - \varepsilon_2 + R_2 i_2 = 0 \end{array} \right.$$



**KAPITAŁ LUDZKI**  
NARODOWA STRATEGIA SPÓJNOŚCI

UNIA EUROPEJSKA  
EUROPEJSKI  
FUNDUSZ SPOŁECZNY



Publikacja współfinansowana ze środków Unii Europejskiej  
w ramach Europejskiego Funduszu Społecznego